

$$i = i_0 \sin \left(\omega t + \frac{\pi}{2} \right)$$

$$\phi = \pi/2 \text{ or } -\pi/2$$

$$\cos \phi = 0$$

$$\text{Power (P)} = 0$$

Current leads the voltage by $\pi/2$

$$i = i_0 \sin(\omega t + \phi)$$

$$Z = \sqrt{R^2 + X_c^2}$$

$$X_c = 1/\omega C$$

$$\tan \phi = 1/\omega CR$$

$$i_0 = E_0/Z$$

- Power factor $\cos \phi = \frac{R^2}{\sqrt{R^2 + X_c^2}}$
- current leading.

$$i = i_0 \sin(\omega t + \phi)$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$X_L = \omega L$$

$$\tan \phi = \omega L/R$$

$$i_0 = E_0/Z$$

- power factor = R/Z
- voltage is leading

$$i = i_0 \sin \left(\omega t - \frac{\pi}{2} \right)$$

Phase difference b/w
 V & I , $\phi = \pi/2$

Power factor
 $\cos(\phi) = 0$

Voltage leads current by $\pi/2$
 $P = 0$

$$i = i_0 \sin(\omega t)$$

$$\phi = 0^\circ$$

$$\cos \phi = 1$$

$$P = V_0 I_0 / 2$$

Current & voltage both are in same phase

$$i = i_0 \sin \left(\omega t \pm \frac{\pi}{2} \right)$$

$$X = X_L - X_C$$

$$\phi = \pi/2$$

- Power factor = 0, Either voltage or current leading

$$i = i_0 \sin(\omega t \pm \phi)$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$X = X_L - X_C$$

$$= \left(\frac{1}{\omega C} - \omega L \right)$$

$$\tan \phi = \left(\frac{1}{\omega C} - \omega L \right) / R, i_0 = \frac{E_0}{Z}$$

